

Pushbuttons, Digital Potentiometer Create Controllable Voltage Output

A digital potentiometer combined with a high-voltage switching regulator and two pushbuttons creates a controllable, variable-output voltage source.

In some applications, it's necessary or convenient to control a voltage using a pushbutton switch. With the circuit described in this article, an output up to 20 V can be controlled simply and efficiently with a pushbutton digital potentiometer. The solution represents an adjustable power supply and can be used in various applications where adjustable voltage output is required.


The circuit (Fig. 1) is based on a switching regulator with variable output power, using the [AD5116](#) digital potentiometer (sometimes called a digiPOT, a digitally controlled potentiometer, or a DCP) and the [ADCMP371](#) comparator with an integrated push-pull output stage. (Note that by adding a switch instead of the pushbutton, the voltage can be adjusted by a microcontroller.) The AD5116 has 64 possible wiper positions with an end-to-end resistance tolerance of $\pm 8\%$ along with an EEPROM to store the wiper position, which can be set manually via a pushbutton. This function is helpful in ap-

plications that require a fixed or known position on power-up.


The circuit is supplied by the voltage V_{IN} , which can be up to 20 V. Supply voltage V_{DD} for the AD5116 and the ADCMP371 can also be generated by V_{IN} ; for example, via a voltage regulator such as the [ADP121](#).

In operation, output voltage V_{OUT} is controlled via the switching frequency of the feedback network. It's fed back to the comparator via a voltage divider and then compared with the reference voltage set by the digital potentiometer. If the voltage derived from V_{OUT} is higher than the reference voltage, the comparator output goes low, thereby blocking both NMOS transistor T1 and the PMOS transistor T2, which decreases V_{OUT} . If the voltage derived from V_{OUT} is lower than the reference voltage, the comparator output switches to high and the two transistors switch to their conductive state (saturation), which increases V_{OUT} .

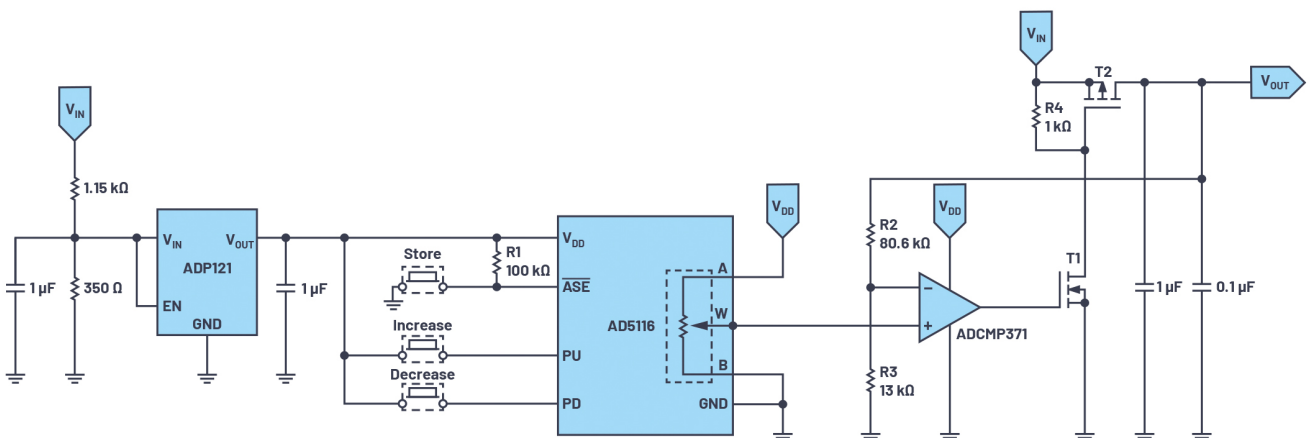Through this comparison-based function, the transistors



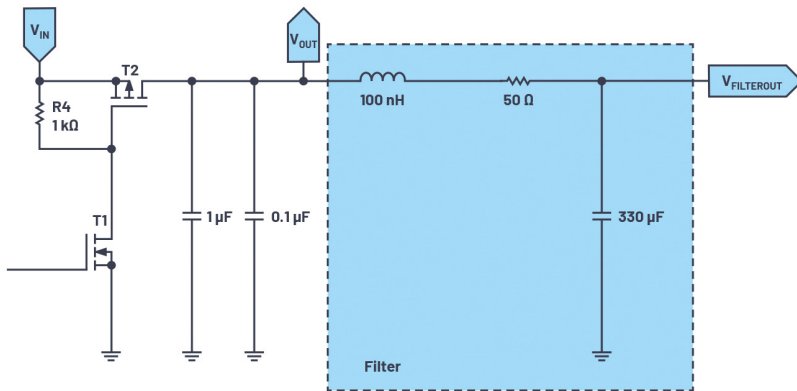1. Combining a digital potentiometer with a high-voltage switching regulator creates a pushbutton-controlled, variable-output voltage source.



2. A filter circuit is required to smooth the output voltage; there are several tradeoffs in filter-component selection.

operate in on-off switching mode with short pulses, which keeps the respective transistor losses low. The switching frequency is influenced by the load at V_{OUT} , in addition to the output voltage of the potentiometer.

As the digital-to-analog converter (DAC) output voltage increases, T2 is off for a longer time and the comparator output is accordingly high. The comparator output delivers a series of faster positive-output pulses with a higher frequency. The reverse occurs when the DAC output voltage is decreased. The filtered V_{OUT} is determined via Equation 1:

$$V_{OUT} = V_W \times \left(1 + \frac{R_2}{R_3}\right) \quad (1)$$

where V_W is the DAC output voltage at the potentiometer tap W.

The resistance between tap A and tap B on the AD5116 is nominally 5 kΩ and divided into 64 steps. At the lower end of the scale, the typical wiper resistance R_W drops to 45 Ω to 70 Ω. The output voltage at V_W in relation to GND is

$$V_W = \frac{R_{WB}}{R_{AB}} \times V_A \quad (2)$$

whereby R_{WB} yields:

$$R_{WB} = \frac{D}{64} \times R_{AB} + R_W \quad (3)$$

where R_{WB} is the resistance value between tap W and GND on the lower scale, and R_{AB} is the total resistance of the potentiometer. V_A is the voltage at the upper end of the divider string (in this case, it's equal to V_{DD}) where D is the decimal equivalent of the binary code in the R_{DAC} register of the AD5116. The R_{DAC} register of the AD5116 is controlled with the pushbuttons PD and PU. A default position—for example, $V_{OUT} = 0$ V on power-up—can be stored in the EEPROM of the potentiometer via the ASE pin.

An additional filter is used to smooth output voltage V_{OUT} and reduce the ripple, which is caused by the switching of T1 and T2 (Fig. 2). The maximum and minimum switching frequencies and the operating voltage range of the AD5116 should be considered in the design of this filter.

For the circuit shown, the switching frequency is in the range of about 1.8 to 500 Hz. Because this is quite low, relatively large values of R, L, and C are normally required for dimensioning the filter cutoff frequency. However, the series resistor of the filter and the output load form a voltage divider, which reduces the output voltage. For this reason, R should be selected to be relatively low.

A simple RLC low-pass filter was implemented in the circuit with R, C, and L values of 50 Ω, 330 μF, and 100 nH, respectively. As an alternative option, the circuit can be constructed with a pulse width modulator (PWM) to drive the transistors and an upstream error amplifier.

Thomas Brand began his career at Analog Devices in Munich in 2015 as part of his master's thesis. After graduating, he was part of a trainee program at Analog Devices. In 2017, he became a field applications engineer. Thomas supports large industrial customers in Central Europe and specializes in the field of industrial Ethernet. He studied electrical engineering at the University of Cooperative Education in Mosbach before completing his postgraduate studies in international sales with a master's degree at the University of Applied Sciences in Constance.

References

Analog Devices, [CN-0405: High Voltage Output DAC with Push-Button Control](#) (2017)
 Analog Devices, [“Choosing the Correct digiPOT for Your Application”](#) (2018)
<https://www.analog.com/media/en/news-marketing-colateral/solutions-bulletins-brochures/choosing-the-correct-digipot-for-your-application.pdf>