

Reliable Power Switch for Privacy Apps Has Offline Memory

The circuit described in this article, essentially a replacement for a mechanical switch, isn't connected to the gadget's processor, making it impossible to hack in and turn on/off the camera and/or microphone remotely.

Today, privacy concerns are being raised more often than ever before. Big tech companies are constantly being accused of secretly gathering users' personal information and even selling it to third-party entities.

In times when nearly every household has at least one gadget with a camera and microphone, besides smartphones, people start thinking twice about the trust they give to the manufacturer and service provider before buying another device. A huge number of cases involve cameras that were hacked and controlled remotely. People began installing external camera covers and taping a microphone hole.

To solve this problem, a mechanical toggle switch can be installed on a camera/mic by the manufacturer, ensuring protection against hackers as well as serving as a visual indicator of the on/off state. However, the downside is the bad design and ergonomics of such solutions.

The circuit described in this article is designed for devices that need to prioritize privacy. For example, in gadgets with a camera and/or microphone, the user has to be sure that the camera (microphone) is turned off if desired, even after the gadget was powered off and on again for a long period. Also, if someone with bad intentions wants to hide the fact that the camera (microphone) is on by removing the LED indicator (or shortening it), the camera (mic) will be turned off automatically.

The circuit isn't connected to the gadget's processor, making it impossible to hack in and turn on/off the camera and/or microphone remotely.

Essentially, this circuit is a replacement for the mechanical toggle switch; however, it uses a tiny pushbutton that allows for easy integration into the gadget's design. See the block diagram in *Figure 1* and the [Go Configure Software Hub's](#)

GreenPAK Designer project in *Figure 2* (the design file is [available here](#)).

Design Operation: Schematic Design

The [AnalogPAK SLG47004](#) has two digital rheostats that can be configured as one digital potentiometer. One of its features is the ability to store its value after powering off. This feature is used in the current design as a 1-bit memory cell. Each time the button is pressed, the potentiometer RH0RH1 changes its value from 0 to 1023 or 1023 to 0, depending on the previous state.

As a result, voltage changes on the middle tap (Pins 7 and 8) from 0 to VDD and vice versa, making it a simple switch that controls an internal power P-FET. In turn, it's used to output the voltage to an external device. The switch is capable of delivering up to 300 mA.

The digital potentiometer (made from RH0 and RH1) has built-in memory with 1,000 cycles, which may not be enough for a long period of device usage if every button is pressed one cycle. Thus, in this design, the memory writing sequence occurs only when the gadget (the main device that includes this circuit) is powered off. For this purpose, the ACMP0L is used as a voltage drop detector.

If the power-source voltage drops below 4.5 V, the ACMP will trigger the CNT3/DLY3 to form the "program" pulse initiating the memory writing sequence. Both VDD pins are connected to the source through the Schottky diode and together with the 2.2 μ F capacitor to delay power off. Therefore, even if the source voltage drops rapidly to 0, the VDD voltage will slowly decay, leaving enough time for the memory writing sequence to complete (*Fig. 3*).

To measure the time required for the program sequence,

a simple setup was used. It's known that the current consumption significantly increases during the erase and write procedure. Thus, the power supply to the IC was connected through a 1-kΩ resistor with oscilloscope probes connected to it.

As can be seen in *Figure 4*, the program time for both rheostats is 25.28 ms, and the current during the process is about 1 mA. It should be noted that these values depend greatly on the voltage level, room temperature, and other factors. The program time may increase two to three times. So, the power-off delay must be longer than that.

The program procedure starts when VDD drops below 4.5 V, and it should end at no less than 2.5 V (see the datasheet). The 2.2-μF capacitor ensures a long enough power-off delay with room to spare (*Fig. 3, again*). Note that the capacitor type should be chosen with low leakage.


Also, since the potentiometer is connected between VDD

and GND, there will be a constant current flowing through it:

$$5 \text{ V} / 100 \text{ k}\Omega = 50 \mu\text{A}$$

That's an order of magnitude more than the quiescent current of the SLG47004. To reduce overall current consumption, the Wake and Sleep (W&S) timer is used. It's set to 1:100, meaning that the current will flow through the potentiometer only once in a hundred of clocks of the OSC0. Approximately 0.49-ms wake and 49-ms sleep. As a result, the device's quiescent current described here is close to 3 μA in an off state, making it perfect for battery-operated gadgets.

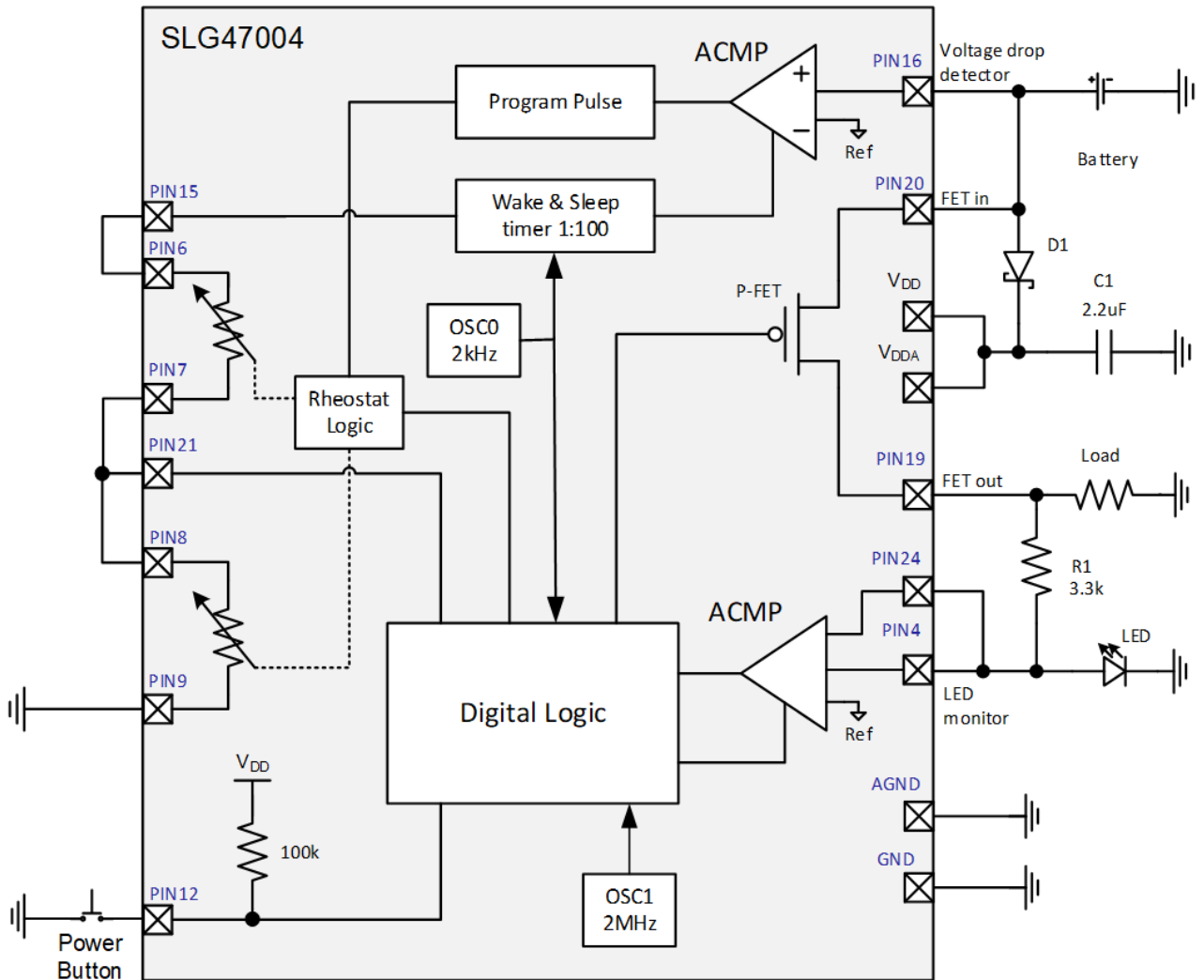As previously mentioned, the designed device is equipped with an LED monitor. Two op amps configured as ACMPs are used for this purpose. OPAMP0 senses the LED brake and OPAMP1 senses the LED short circuit. In both cases, it switches off the P-FET and powers down the load (camera/



1. This circuit can replace the mechanical toggle switch; it uses a tiny pushbutton that allows for easy integration into the gadget's design.

mic). Also, both op amps are enabled only when the switch is on, helping to save the battery in an off state.

This design also is equipped with an internal button to debounce delay (CNT2/DLY2), instead of the typical external RC filter in such cases.

Design Operation: Macrocells

Pin12 is configured as a digital input with Schmitt trigger that has a 100k pull-up resistor. It serves as an input for the pushbutton (Fig. 1, again). Then the signal goes through the 30-ms debounce delay (CNT2/DLY2), triggering the 1.46-ms one shot (CNT1/DLY1). This starts the OSC1 (2.048 MHz), forming a Write Window with a series of pulses to change the state of the potentiometer RH0RH1. See the oscilloscope screenshot in Figure 5.


OSC0 serves as a clock for all counter-delays in this design. Since it has very low power consumption (0.44 μ A), it's set to Force Power On.

As mentioned in the "Schematic Design" section, the

SLG47004 has two rheostats—in this project, they're configured as one digital potentiometer. Its upper and lower pins (Pins 6 and 9) are connected in between ground and Pin 15, which is an output for the W&S timer. The middle tap (Pins 7 and 8) is connected to Latch 1 through a digital input with Schmitt trigger Pin 21.

Latch 1 latches the potentiometer state during sleep mode (using an inverted W&S signal), making an appearance as if the potentiometer is constantly connected to VDD but consuming 100X less current. After the latch, the signal goes to a potentiometer's Up/Down input through a 2.44-ms delay (CNT5/DLY5) needed for the pot to settle in. This signal flips the potentiometer's count up or down with every next write window. Simultaneously, the signal goes through the filter (filtering a 20-ns spike appearing due to the latch's lag) to 2-bit LUT3. The LUT controls the output power P-FET (Pins 19 and 20).

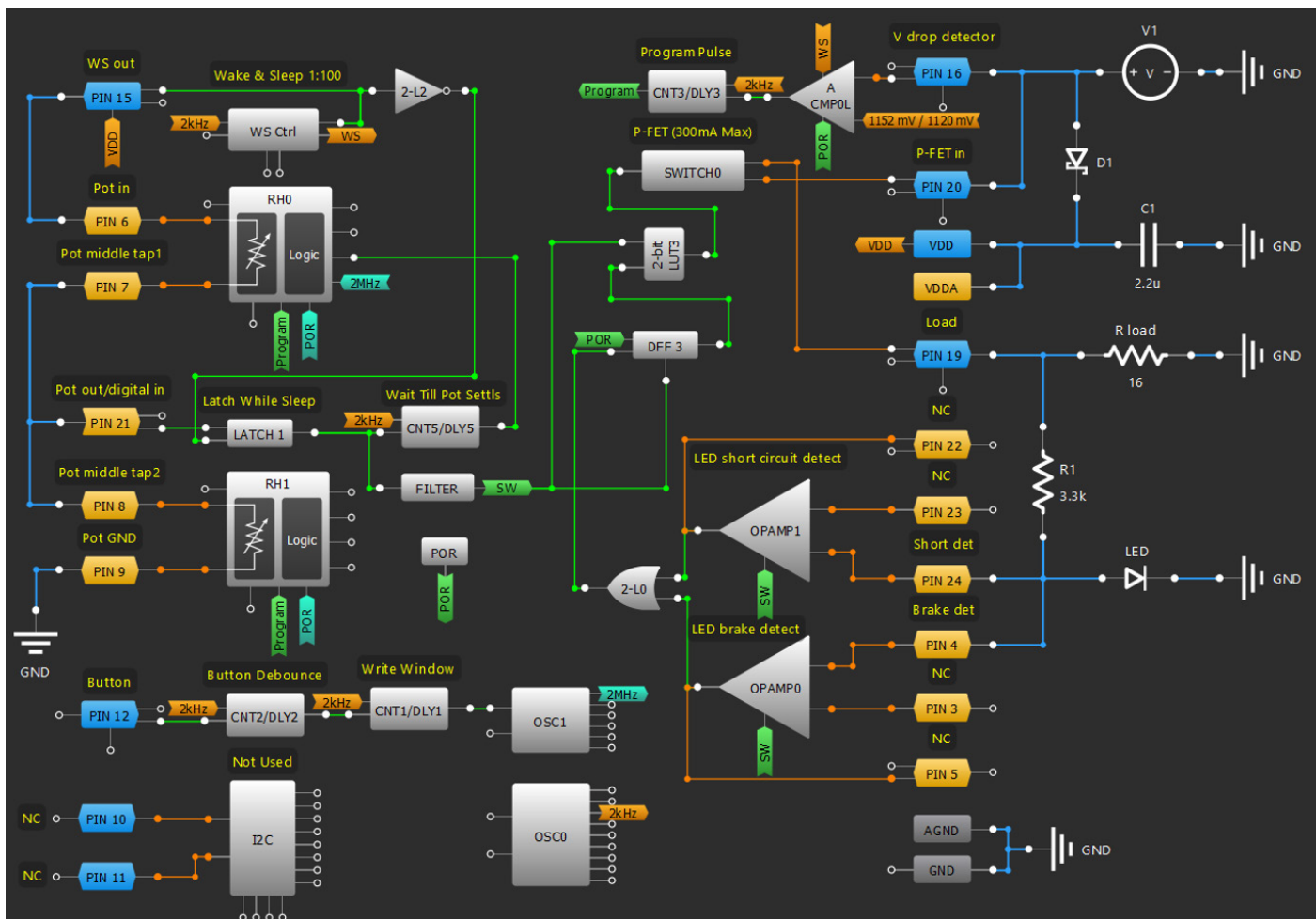The LED monitor consists of OPAMP0 and OPAMP1 and analog inputs Pins 4 and 24. It detects the LED's short circuit



2. The GreenPAK Designer Project.


or circuit break, and with the help of 2-bit LUT0, DFF3 shuts down the P-FET if the LED malfunctions.

The Wake and Sleep timer (WS Ctrl) plays an important role in saving energy if the device is battery-operated. Since this project uses analog macrocells that are the most “energy-hungry,” the W&S makes it possible to save energy by powering on those macrocells for a short period of time.


The wake-to-sleep ratio is set to 1:100.

The CNT3/DLY3 together with ACMP0L start the pot’s “program sequence” as described in the Schematic Design section (see Fig. 1 and the oscilloscope screenshots in Fig. 3).

 
It should be noted that the I²C macrocell along with its Pins 10 and 11 are used only to program the chip during production and should not be used during device operation.



 3. Voltage drop detection and program pulse.



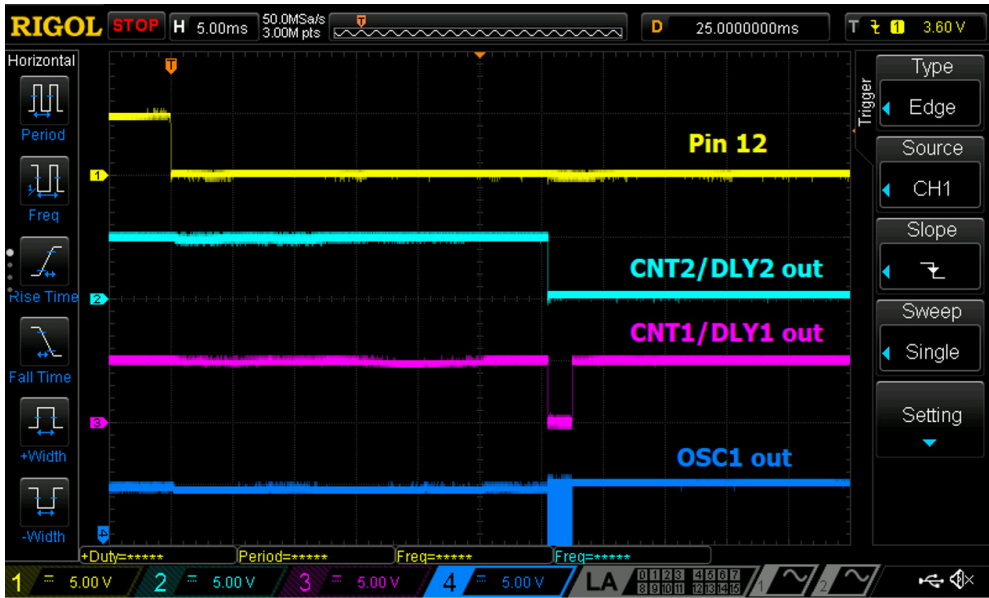4. Voltage drop during program procedure.



5. Write window.

Pins 10 and 11 should be left unconnected on the PCB.

Tables 1-11 below provide specifications on the different elements involved in the macrocell's configuration.

Conclusion

The circuit described in this article functions like a mechanical toggle switch, but uses a micro pushbutton that can be easily integrated into the gadget's design. The power switch has a memory akin to a mechanical switch, meaning if the user turned it off, it stays off.

In this design, an LED is used as a power indicator. It has fault protection, so if the LED is not glowing for any rea-

son, the load (camera/mic) will also be off, ensuring desired privacy protection. In addition, in an off state, the device has a very low current consumption of approximately 3 μ A, which is perfect for most battery-powered devices.

Table 1. PINs

Properties	PIN μ to 9, 16, and 20, 22 to 24	PIN 19	PIN 10 and 11	PIN 12	PIN 15	PIN 21
I/O selection	Analog input/output	Analog input/output	Digital input	Digital input	Digital output	Digital input
Input mode OE=0	Analog input/output	Analog input/output	Digital in without Schmitt trigger	Digital in with Schmitt trigger	None	Digital in with Schmitt trigger
Output mode OE=1	Analog input/output	Analog input/output	None	None	1x push pull	None
Resistor	Floating	Pull Down	Floating	Pull Up	Floating	Floating
Resistor value	Floating	1M	Floating	100K	Floating	Floating

Table 2. FILTER/EDGE DETECT

FILTER/EDGE DET	
Type	FILTER
Output polarity	Inverted (nOUT)

Table 3. LUT

IN1	IN0	2-bit LUT0	2-bit LUT2	2-bit LUT3
0	0	0	Inverter	0
0	1	1		0
1	0	1		1
1	1	1		0

Table 4. DFF/LATCH

Properties	2-bit LUT1/DFF/LATCH1	3-bit LUT0/DFF/LATCH3
Type	DFF/LATCH	DFF/LATCH
Mode	LATCH	DFF
Second Q select	--	Q of first DFF
nSet/nReset option	None	nRESET
Initial polarity	Low	Low
Q output polarity	Inverted (nQ)	Non-inverted (Q)
Active level for RST/SET	--	Low level

Table 5. Oscillators

Properties	OSC0	OSC1
Control pin mode	Power down	Power down
OSC power mode	Force Power On	Force Power On
Clock selector	OSC	OSC
CLK predivider by:	1	1
OUT0 second divider by:	1	1
OUT1 second divider by:	1	1

Table 6. Digital Rheostat

Properties	RH0	RN1
Mode	None	Potentiometer
Charge Pump Enable	From matrix	From matrix
Charge Pump Clock	Auto selection	Auto selection
Auto-Trim	Disable	--
Active level for UP/DOWN	Up when LOW	--
Resistance (initial data)	0	--
UP/DOWN source	Ext. (From matrix)	--
Clock	Ext. Clock (From matrix)	--

Table 7. Analog Switch

Properties	SWITCH0
Mode	Analog Switch
Big PMOS control	By Matrix
Small NMOS enable	Disable
Half Bridge Dead Time Select	Bypass

Table 8. CNT/DLY

Properties	16-bit WS Ctrl (MF0)	8-bit CNT1/DLY1 (MF1)	8-bit CNT2/DLY2 (MF2)	8-bit CNT3/DLY3 (MF3)	8-bit CNT5/DLY5 (MF5)
Multi-function mode	CNT/DLY	CNT/DLY	CNT/DLY	CNT/DLY	CNT/DLY
Type	Wake sleep controller	--	--	--	--
Mode	--	One shot	Delay	One shot	Delay
Counter data	100	2	61	1	4
Edge select	High level reset	Falling	Both	Falling	Both
DLY IN init. value	Bypass the initial	Bypass the initial	Bypass the initial	Bypass the initial	Bypass the initial
Output polarity	Non-inverted (OUT)	Inverted (nOUT)	Non-inverted (OUT)	Non-inverted (OUT)	Non-inverted (OUT)
ACMP0L wake sleep	Enable	--	--	--	--
ACMP1L wake sleep	Enable	--	--	--	--
At OSC0 power down	Force sleep (Low)	--	--	--	--
ACMP0L wake time selection	Short wake time	--	--	--	--
ACMP1L wake time selection	Short wake time	--	--	--	--
Up signal sync	Bypass	--	--	--	--
Keep signal sync	Bypass	--	--	--	--
Mode signal sync.	Bypass	Bypass	Bypass	Bypass	Bypass
FSM SET/RST Selection	Reset to 0	--	--	--	--
Clock	OSC0	OSC0	OSC0	OSC0	OSC0

Table 9. ACMP

Properties	ACMP0L
IN+ gain	x0.25
Vref LPF	Disable
Low power start up	Disable
Sampling mode	Disable
Vref source selection	2.048 V
Connections	
IN+ source	PIN 16 (GPIO2)
IN- Low to High source	1152 mV
IN- Low to Low source	1120 mV

Table 10. OPAMP

Properties	OPAMP0	OPAMP1
Mode	ACMP mode	ACMP mode
Bandwidth Selection	128 kHz	128 kHz
Charge Pump	Enable CP	Enable CP
Supporting Blocks On/Off	Follows OPAMP	Follows OPAMP
Vref connection	To IN+	To IN-
Vref	1024 mV	VDDA * (50 / 60)

Table 11. VREF

Properties	VREF OPAMP0	VREF OPAMP1
Enable selection	From register	From register
Register enable	Dynamic On/Off	Dynamic On/Off
Input voltage selection	VDDA	2.048 V
Output selection	VDDA * (50 / 60)	1024 mV