

# How to Push ADAS Processors Beyond 100 A While Ensuring Functional Safety

**Sponsored by Texas Instruments: Functions ranging from parking assistance to full autonomous driving require multicore processors powered by buck converters that can safely deliver high currents while minimizing EMI.**

Vehicles are taking on an increasing number of advanced capabilities, including adaptive cruise control, forward collision warning, automatic high-beam control, driver monitoring, parking assistance, vehicle-to-everything (V2X) communications, and full autonomous driving. As vehicles offer more and more of these features, they require considerable processing power, and modern advanced driver-assistance systems (ADAS) can draw in excess of 100 A.

Choosing the processors and power supplies that deliver the necessary voltages and currents while minimizing electromagnetic interference (EMI) can present challenges.

## ADAS System-on-Chip

[One processor suitable for use in ADAS applications is Texas Instruments' TDA4VH-Q1 automotive system-on-chip \(SoC\).](#) Combining eight Arm Cortex-A72 application cores, it offers depth-and-motion, video-encode/decode, vision-preprocessing, and deep-learning hardware accelerators. To help you pinpoint the exact current and voltage requirements of your specific TDA4VH-Q1 application, TI offers a power-estimation tool.

After determining the requirements of your specific ADAS, you can use TPS62876-Q1 buck converters to deliver the necessary power. These converters come with maximum current ratings from 15 to 30 A, but they offer a stacking feature that enables them to work together to provide currents beyond 100 A.

*Figure 1* shows two TPS62876-Q1 devices in a stacked

configuration. Here, the lower device operates in secondary mode, programmed by tying its SYNC\_OUT pin to ground. For optimal current sharing in stack mode, both devices should operate at the same switching frequency, as programmed via each device's FSEL pin.

Other features of the TPS62876-Q1 include droop compensation, which improves load-transient tolerance while minimizing the required output capacitance to reduce cost and improve power density. The devices also have a remote-sensing capability that lets them power SoCs with tight power-supply voltage tolerances.

In addition, a spread-spectrum clocking function helps to minimize EMI by modulating the switching frequency  $\pm 10\%$  around the nominal value. Finally, the devices can report overtemperature and overcurrent warnings over their I<sup>2</sup>C interfaces.

Of course, functional safety is a critical aspect of ADAS and other automotive applications. The TPS62876-Q1 falls into TI's Functional Safety-Capable product category and comes with documentation that addresses failure-in-time rates and component failure modes.

## Dual-Phase Step-Down Converter


[An alternative is to use a device in the TPS6288x-Q1 family of dual-phase step-down converters](#) (*Fig. 2*). These converters are available with 12-, 20-, 24-, and 30-A ratings and have a stacking feature that enables five devices to operate in parallel; thus, you can deploy five of the 30-A TPS62883-Q1 versions for a total 150-A rating. The input voltage range



able up to four phases.

The LM5137F-Q1 has several features that help minimize EMI and facilitate compliance with relevant EMI standards. It includes adaptively timed high-current MOSFET gate drivers that minimize EMI at high input voltages and switching frequencies while also reducing switching losses. The two-output configurations support 180-degree interleaved operation to reduce input-capacitor ripple current and EMI filter size.

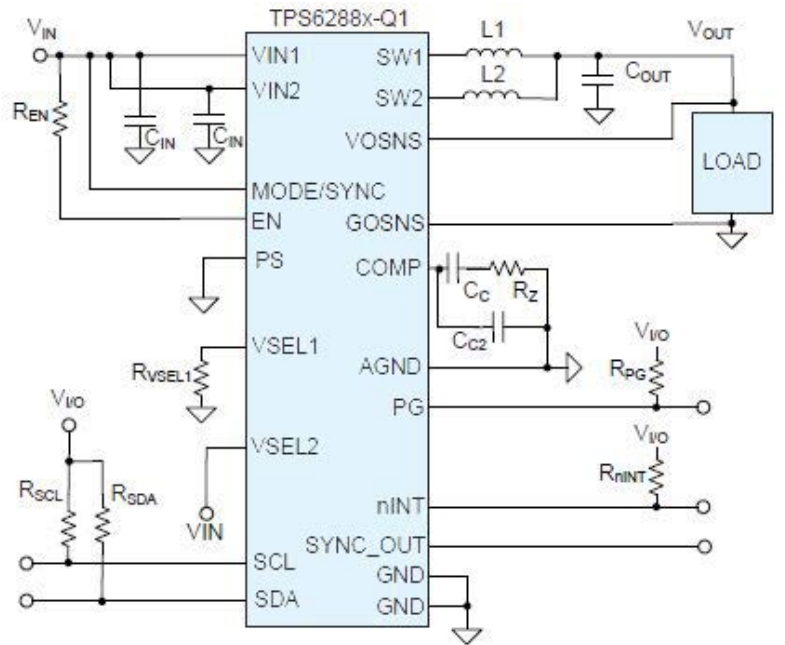In addition, the controller includes a programmable, dual-random, spread-spectrum function, and its resistor-adjustable switching frequencies can be synchronized to an external clock to eliminate beat frequencies. Like the TPS6288x-Q1, the LM5137F-Q1 supports functional-safety designs up to ASIL D.




2. The TPS6288x-Q1 family of dual-phase buck converters minimize voltage ripple and inductor size.

### Buck Controller Evaluation Module

To help you get started with the LM5137F-Q1, TI offers the LM5137F-Q1-EVM12V evaluation module (EVM), which operates over a 36- to 72-V input range and delivers a 12-V, 20-A output. You can customize the output voltage from 3.3 to 20 V by altering feedback-

resistor values. The module comes with an electrolytic capacitor for parallel damping and an input  $\pi$ -stage EMI filter.

Figure 3 shows a recommended test setup for the EVM. TI recommends using voltmeters with input impedances of

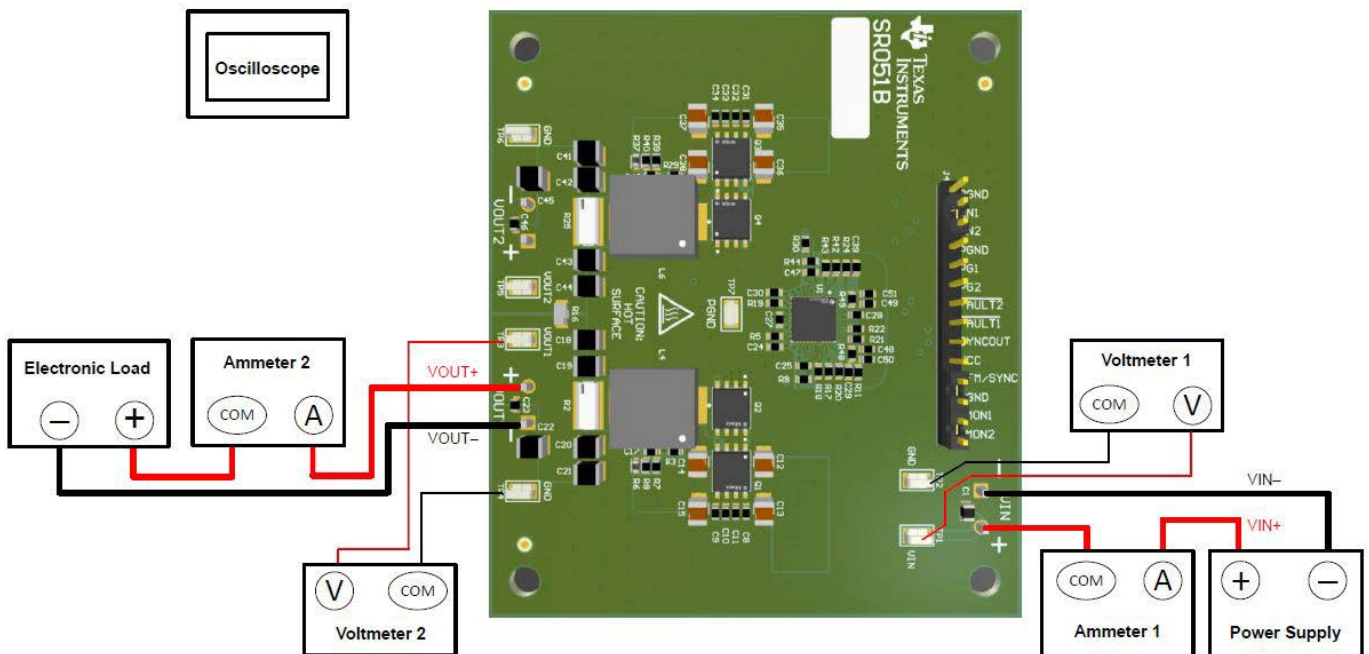

3. A simple test setup lets you investigate input and output DC voltages and currents as well as output voltage ripple.

100 M $\Omega$  and setting ammeter aperture times to 1 second. To measure output voltage ripple, use a 20-MHz oscilloscope in AC-coupling mode, place the scope probe on the positive terminal of the output capacitor, and connect the probe ground lead to the capacitor's negative terminal.

### **Conclusion**

As increasingly sophisticated vehicles take on more advanced driver-assistance features extending all the way to autonomous operation, they require ADAS that can draw in excess of 100 A. TI offers a lineup of buck converters and controllers that can deliver the necessary currents while minimizing EMI and meeting functional-safety requirements. The company also offers evaluation modules that can help you get started and keep your designs on the right track.