

Power Sequencing, Simplified

A new approach to power sequencing doesn't require any programming, digital communication, or even a bias power supply.

From [graphics processor units \(GPUs\)](#) and central processing units (CPUs) to [field-programmable gate arrays \(FPGAs\)](#), digital signal processors (DSPs), and [heterogeneous SoCs](#), every processor requires power sequencing. These digital loads often operate from multiple voltage rails, each of which may supply a different on-chip power domain. [Power sequencing](#) is the process of applying and removing power from these voltage rails in a specific order during system startup and shutdown.

If the appropriate sequencing isn't followed, the function of the load may be limited and defective. Also, in extreme cases, the load can be destroyed. To prevent this, sequencing functions are employed.

This article discusses different possibilities for the implementation of a sequencing and voltage-monitoring function. It also introduces a new, simple-to-use sequencing solution that requires no programming, digital communication, or bias power supply. These features are important

because the sequencer itself needs to be powered on first in a system. By that time, processors or other loads usually aren't running yet.

How Power Sequencing Typically Works


One common approach to sequencing involves placing several [DC-DC converters](#) in front of the processor and switching them on one after the other by linking the generated voltages with [enable \(EN\) pins](#). One drawback with this approach is the requirement of [voltage regulators](#) with an exact definition of the precision enable pin. The other drawback is that a fixed sequence of switch-off of the individual voltages is difficult to implement. Also, the exact time course can only be implemented with additional cumbersome circuitry.

Given all that, a dedicated sequencing controller is often preferred. *Figure 1* outlines such a system. The voltage converters — from the first, DCDC1, to the last, DCDC n — are switched on and off by a sequencer in the correct order through the respective enable pins.

Ideally, the sequencing circuit should support a [wide input voltage range](#) since it needs to perform its function before the respective voltages in the system are switched on. Thus, a wide operating input voltage range is favorable.

The sequencing function can be implemented in several different ways. A [microcontroller \(MCU\)](#), a small FPGA, a dedicated programmable power sequencer, or a simple sequencer could be used, depending on the complexity and flexibility required.

 Many of these solutions have unfavorable limitations. The MCU must first power up and execute its firmware be-



1. DC-DC converters supplying loads with multiple voltage rails need to coordinate their power-up and power-down sequences to ensure proper system operation. Analog Devices

fore it's able to perform the sequencing function. A small control FPGA or a programmable power sequencer must be programmed before operation. This can be completed before the device is soldered onto the PCB or after assembly, prior to the system's initial power-up. In both cases, the additional programming step can lead to considerable effort and costs.

A New, Simple-to-Use Approach to Power Sequencing
An alternative approach eliminates the need for programming in production. In this type of sequencing solution, timing and operating behavior are configured using only external resistors and capacitors. With a very wide input voltage range of 2.7 to 15 V, this sequencer can be operated directly from a 3.3-, 5-, or even 12-V supply voltage without

SYSTEM DESIGNERS must contend with the increasing complexity of power sequencing. Today's electronic systems need more power density, with the number of voltage rails growing at both the chip and system levels.

Today's processors are more heterogeneous than ever. Everything from CPU cores are crowding onto the same silicon die as on-chip accelerators, such as GPUs and NPU's, as well as memory controllers, high-speed SerDes, and I/O interfaces like PCIe. Each of these sub-systems may require a different supply voltage to run efficiently.

To manage this complexity, chip designers partition the processor into independent power domains, often with dedicated voltage rails. This enables fine-grained power management, allowing idle blocks to be completely shut off or dialed down independently to save power.

As a result, a single processor today may contain a dozen or more voltage rails and power domains, while

the complete system can include dozens or even hundreds of interdependent power rails and voltage domains.

Supplying power to all of these rails without considering the power-up and power-down timing for each one poses several dangers. Improper sequencing can cause system failures while increasing the likelihood of long-term damage to the main processor or any of the chips surrounding it, e.g., FPGAs, DSPs, and analog-to-digital converters (ADCs), among many others. One of the primary concerns is the possibility of breakdown in the electrostatic-discharge (ESD) protection and isolation barriers that internally separate two power rails in a chip.

If one rail remains powered while another is inactive for extended periods — or repeatedly experiences these conditions over time — such protections can break down, potentially causing permanent damage to the chip.

